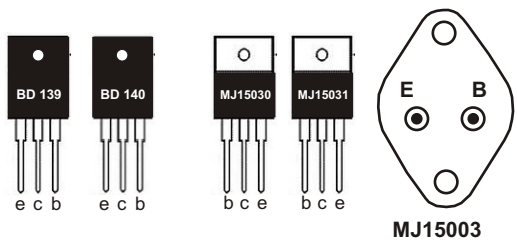


U tačkama "A" i "B" sa milivoltmetrom (opseg 200mV) na osnovu pada napona na otporima **R23** i **R24**, vrši se podešavanje mirne struje izlaznih tranzistora. Vrijednost napona (u mV) treba da bude 5-6mV, bez ulaznog signala (potenciometar Volume na nuli).

www.kesatnet.me
PROJECT Nr: 13



 KesatNet Electronic Praktikum Group Pljevlja - Montenegro	NAME:	
	AUDIO POJAČAVAČ 300W Električna šema	
DATE:	DESIGN:	Nr. P13/ 01
28.02.2011.	Alija Dervić	